

4 Design and simulation of digital circuits using computer aided design software (II)

4.1 Objectives

The management of the libraries is described as means to hierarchy design in Logisim. An example of hierarchy design is detailed. The facilities offered by Logisim for the combinational analysis of a circuit are enumerated.

4.2 Library management in Logisim

An implicit library is attached by default to a Logisim project. The library may contain several circuits represented by their logic diagram. The file created by Logisim – when saving the project – contains the project library with its logic diagrams, as well as the project dependencies. This enables the possibility to load the project library into another project; its circuits will be available for reuse. The integration of circuits from current library or from other libraries is called *hierarchy design*. A library can be loaded with command **Load Library > Logisim-library...** from the **Project** menu. Logisim will request the associated project file, as in Figure 4. 1.

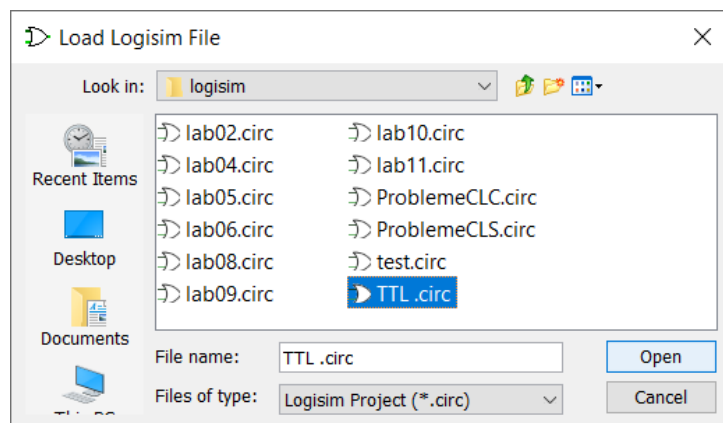


Figure 4. 1 When loading a library, Logisim asks the location of the project file implementing the library

The libraries loaded into the project appear in the Toolbox area, and their circuits – represented by symbols – are available for reuse. Figure 4. 2 highlights the access to circuits from TTL library. A project can load as many libraries as necessary, which allows the possibility to integrate components from multiple sources.

A library can be removed from the project by right-clicking its name and selecting **Unload Library** from the context menu. Selecting **Reload Library** will update the library.

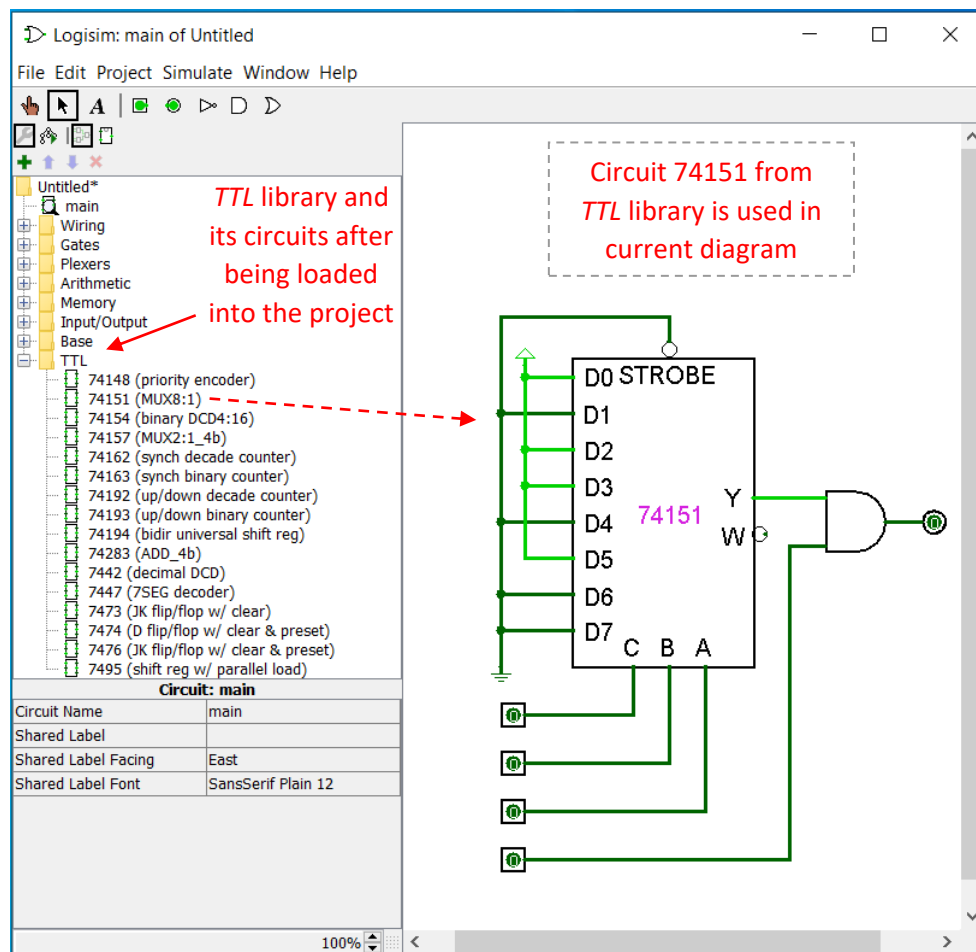


Figure 4. 2 TTL library appears in the Toolbox after being loaded. Its circuits can be accessed via their symbols

4.3 Circuit analysis

A logic diagram supports the following types of analysis:

- Circuit analysis;
- Circuit statistics.

Circuit analysis is available with **Analyze Circuit** command from **Project** menu. The **Combinational Analysis** window that appears when launching this utility is organized on several Tabs as follows (Figure 4. 3):

- **Inputs** – contains the list of input terminals detected on the diagram. They are identified by their label or receive one automatically, if the label is missing.
- **Outputs** – contains the list of detected output terminals.
- **Table** – highlights the truth table of the circuit outputs. A click in the cells of the output columns will toggle the values between 0, 1, and x.
- **Expression** – lists the boolean expressions of the outputs in Minimal Disjunctive Normal Form or in Minimal Conjunctive Normal Form.
- **Minimized** – lists the functions of the outputs in a Minimal Normal Form – sum of products (disjunctive form) or product of sums (conjunctive form) – as set

by the **Format** choice. If the diagram contains up to 4 inputs, this section will highlight the corresponding Karnaugh map. The map has an interactive behavior: any click inside the grid will toggle the value in the corresponding cell between 0, 1 and x. Consequently, the minimization adjusts automatically, with effects on the grouped cells, as well as on the resulting minimal expression. If enabled, the **Set As Expression** button should be pressed, to set the minimized form as primary expression of the Combinational Analysis tool.

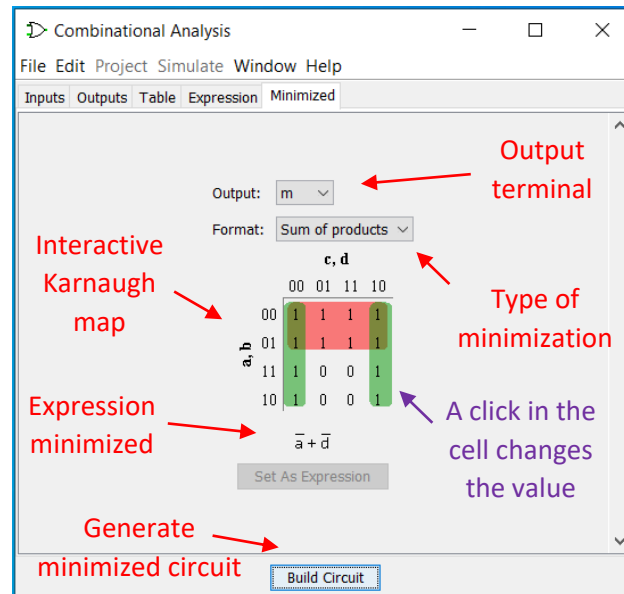


Figure 4. 3 Combinational analysis of the circuit from Figure 4. 4

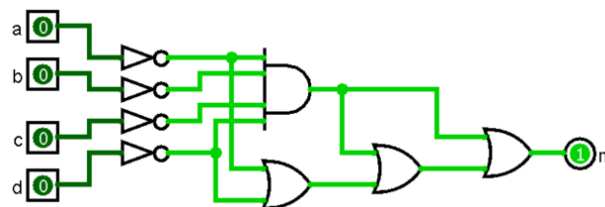


Figure 4. 4 A logic diagram with complex structure that can be simplified using the Combinational Analysis tool

Note: Circuit analysis works only for combinational circuits: which have their outputs as a function of the inputs.

The **Build Circuit** button is available on all tabs of the **Combinational Analysis** window. Pressing the button will generate a new circuit that implements the current expressions in the Combinational Analysis tool. The tool will require the name of the new circuit. The circuit will be attached to the project library. For example, the minimized version of the circuit in Figure 4. 4 is highlighted in Figure 4. 5.

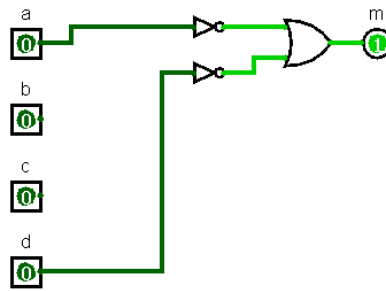


Figure 4. 5 Logic diagram after minimizing the circuit from Figure 4. 4

The Combinational Analysis tool may also be used to generate a new circuit from its analytical expression, truth table or Karnaugh map. When the diagram is empty the tool can be launched with the command **Combinational Analysis** from the **Window** menu. The input terminals may be added in the **Inputs** tab, and the output terminals in the **Outputs** tab. The logic functions corresponding to outputs can be defined analytically in the **Expression** tab, by truth tables in the **Table** tab or through the Karnaugh maps in the **Minimized** tab. **Note:** Karnaugh maps are available if the number of inputs is less than 5. After the output functions are defined, the circuit can be generated by pressing the **Build Circuit** button.

Note: The analytical expression defined in the **Expression** tab accepts the following operators: NOT, AND, OR and XOR. Operator NOT is represented by character \sim , AND is represented by a space, OR can be defined with $+$ and XOR with \wedge . Brackets may also be used if necessary. After finalizing the expression, the **Enter** button should be pressed, if available (Figure 4. 6).


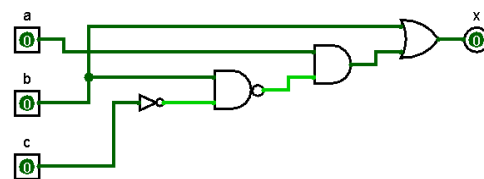
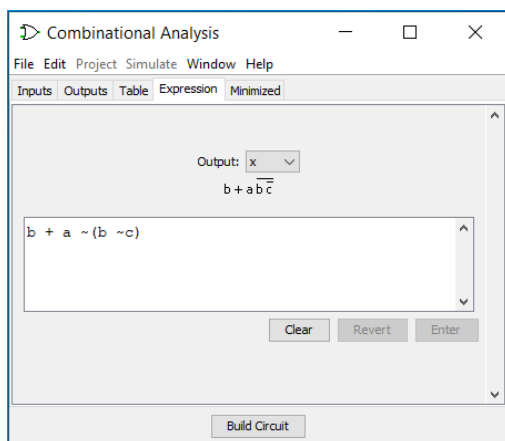


Figure 4. 6 Boolean expression of the output function defined in the Combinational Analysis tool (left). The corresponding circuit generated for this expression (right)

Circuit statistics can be visualized using the command **Get Circuit Statistics** from the **Project** menu. A new window will appear containing statistical data related to elements found in the current logic diagram.

4.4 Assignments

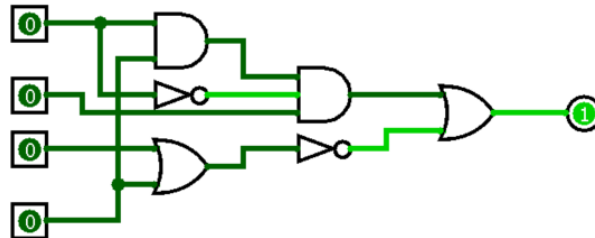1. Create a new project in Logisim and load the *TTL* library. Analyze the list of circuits inside the library.
2. Create a new diagram for the circuit in the next figure and use the Combinational Analysis tool to generate the equivalent circuit obtained after minimization using the **Minimized** tab.



3. Use tabs **Inputs**, **Outputs** and **Expression** from the Combinational Analysis tool to implement the following logic functions in a single logic diagram.

$$f_1 = \sim a + b + \sim c \quad f_2 = \sim(a + b) (a + c) \quad f_3 = \sim a + \sim(\sim b c)$$

4. Implement the logic diagram in the next figure, which represents the design of an unsigned 2-bit comparator unit, using 1-bit unsigned comparators (with attribute Numeric Type=Unsigned) from the *Arithmetic* library, and additional logic gates. Test the 2-bit comparator in the simulator for all input combinations.

The diagram explained: The 2-bit numbers which are compared are A_1A_0 and B_1B_0 . The diagram implements the next rules for the 3 cases possible:

- $F_1 = A_1A_0 > B_1B_0$: $F_1=1$ if $A_1 > B_1$ OR ($A_1=B_1$ AND $A_0 > B_0$);
- $F_2 = A_1A_0 = B_1B_0$: $F_2=1$ if $A_1=B_1$ AND $A_0=B_0$;
- $F_3 = A_1A_0 < B_1B_0$: $F_3=1$ if $A_1 < B_1$ OR ($A_1=B_1$ AND $A_0 < B_0$).

